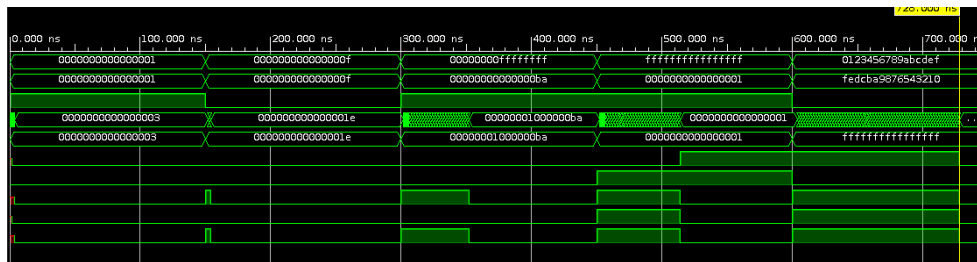



Sample Waveforms:

With delay:

Ripple Carry Adder




2x32 Carry Select Adder

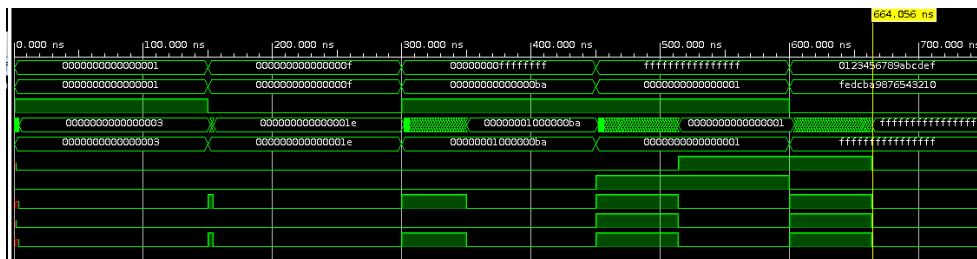


Without delay:

Ripple Carry Adder

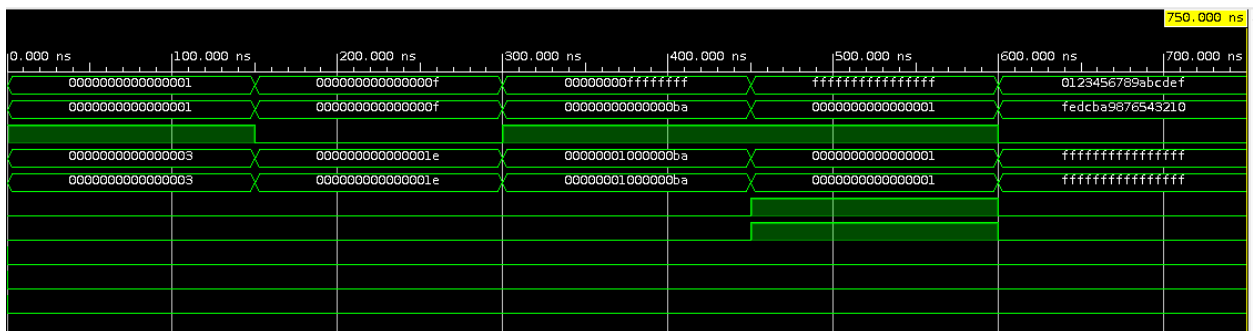


2x32 Carry Select Adder

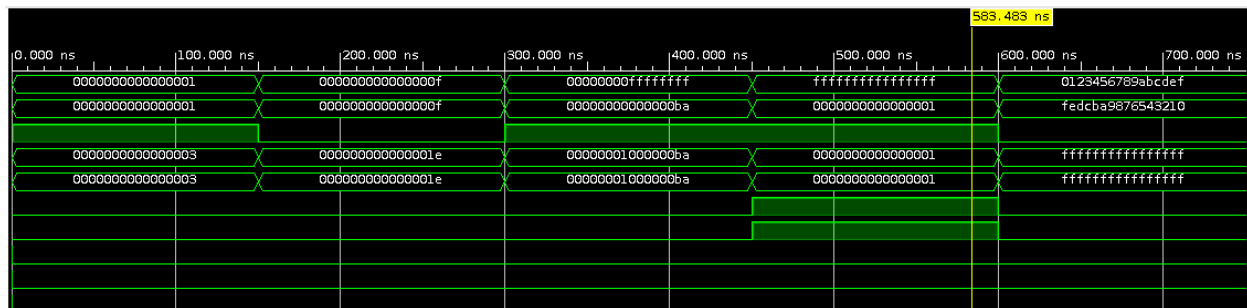


Comparison of longest path delay:

Ripple Carry Adder

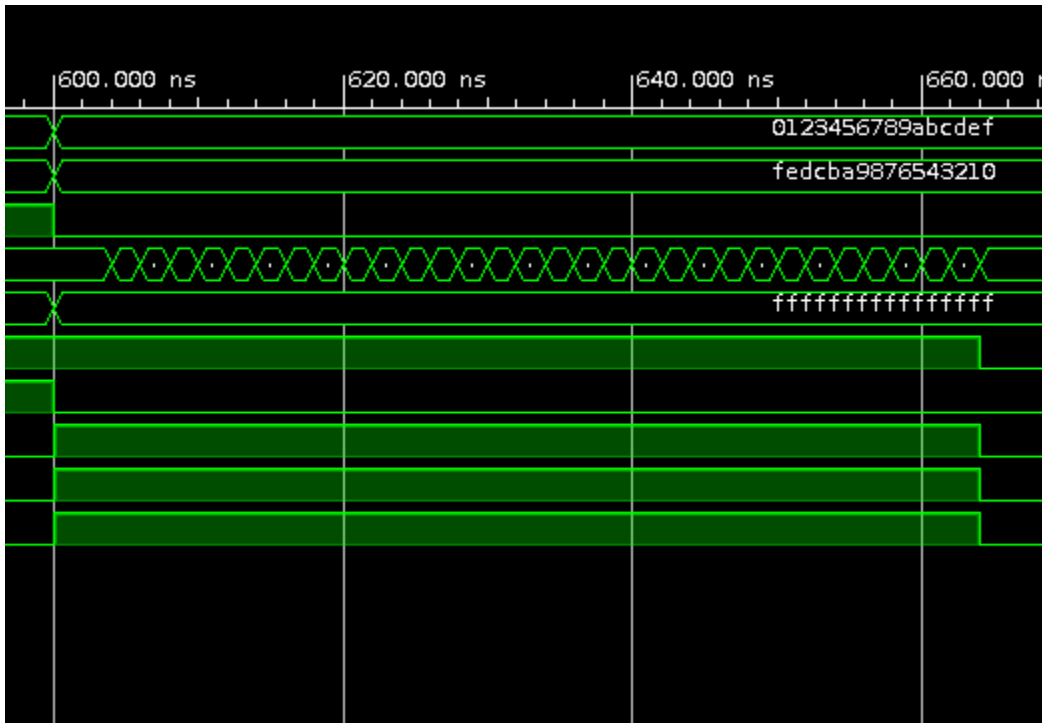


2x32 Carry Select Adder

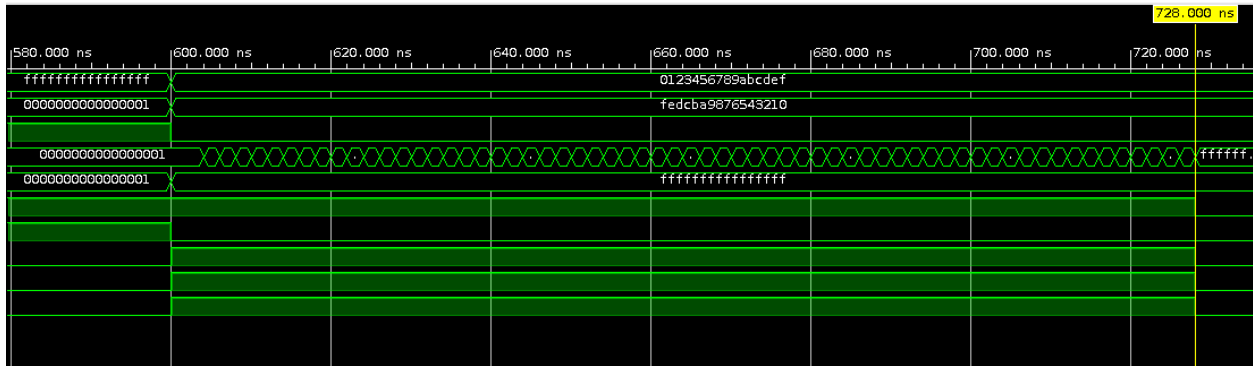Leonardo Mattos Martins
U25267206
Lab 3 Write up



8x8 Carry Select Adder

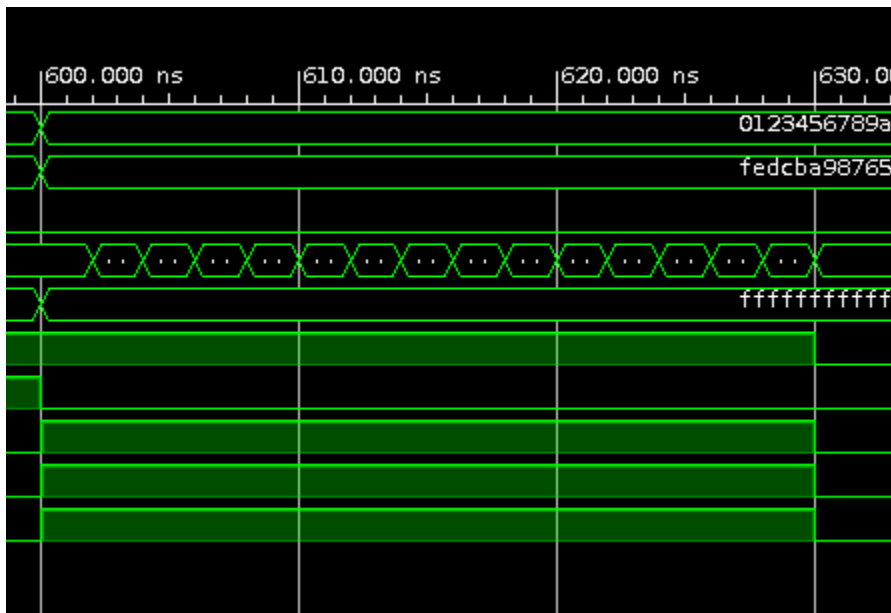

Questions to Answer:

What are the timings of your adders in gate delays?

$$\text{RCA} = 2N$$

$$= 2 * 64$$

$$= 128 \text{ gate delays}$$

$$2 \times 32 \text{ CSA} = 2k + 2(j - 2)$$

$$= 2 * 32 + 2(2 - 2)$$

$$= 64 \text{ gate delays}$$

$$8 \times 8 \text{ CSA} = 2 * 8 + 2(8 - 2)$$

$$= 28 \text{ gate delays}$$

Are they what you expect? Why or why not?

The values above are reflected in the waveforms as the longest path delay. It is also shown how in most cases the bits do not propagate all the way through the adder and the time required is less than what was calculated.

Leonardo Mattos Martins

U25267206

Lab 3 Write up

Explanation of timings: All testbenches use the same conditions to best evaluate their performance against each other. The test cases are: forcing an overall carry out, random large A&B input (w/ and w/o carry), random small A&B input (w/ and w/o carry), random combinations, and the largest amount of delay.